

REPORT ON EXPERIMENT 8

Course No EEE 416

Name : Md Maisoon Rahman

Id : 1606038

Section : A2

Step 1 : Designing the schematic.

In this stage the schematic diagrams were designed based on the lab reference video.

Initially the 8086 part is created while creating the project through project wizard. The following parts were sequentially placed in the schematic capture.

1. 74HC373 2. 8255A 3. 3 seven segment displays

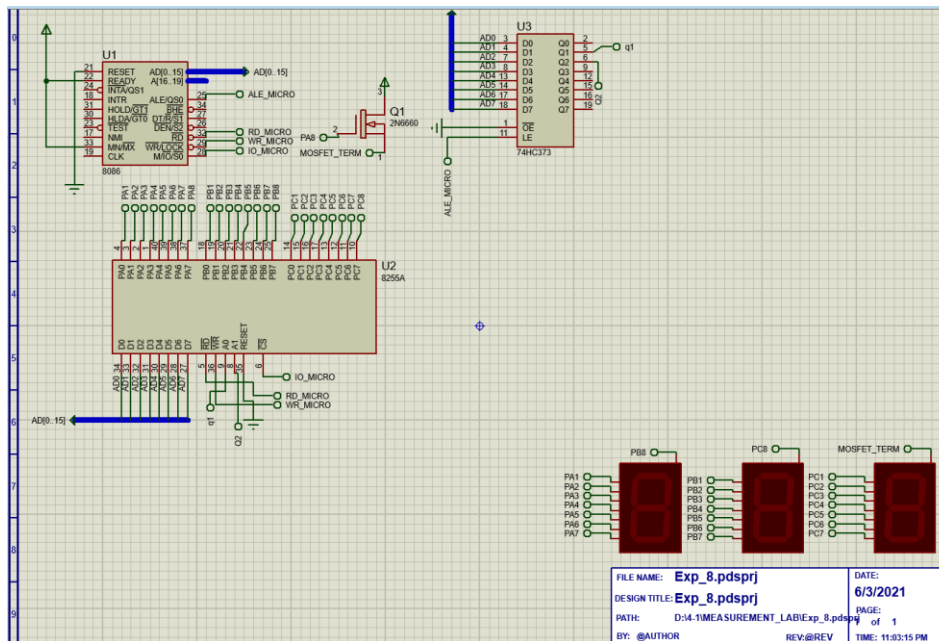


Figure 1 Total schematic layout

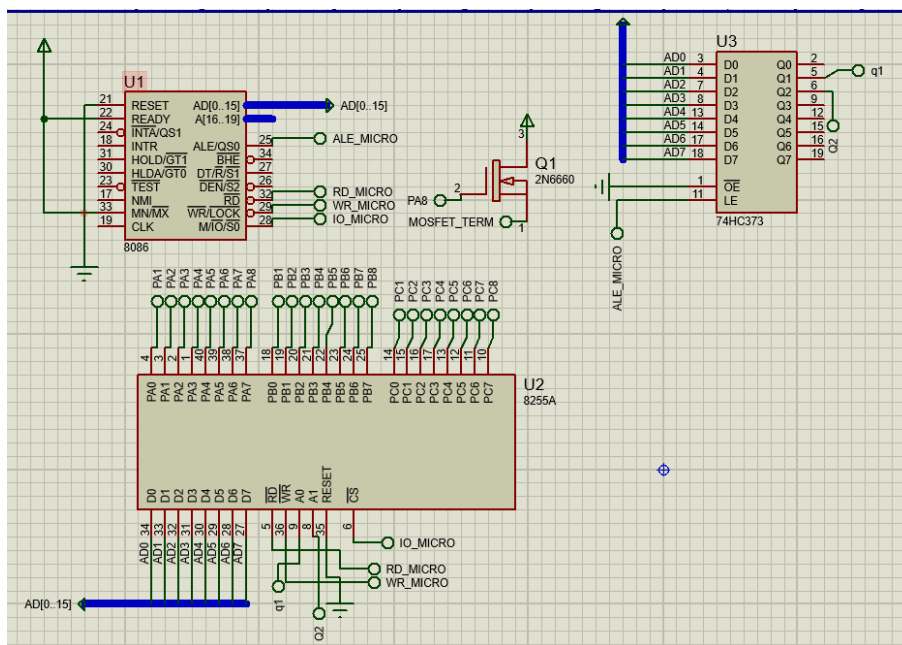


Figure 2 Schematic Capture of the 8255A and 74HC373

Step 2: Creating the source code

Coding for the microprocessor was initially debugged using emu8086.

```
01 ; Main.asm file generated by New Project wizard
02 ;
03 ; Created:   Fri May 28 2021
04 ; Processor: 8086
05 ; Compiler:  MASM32
06 ;
07 ; Before starting simulation set Internal Memory Size
08 ; in the 8086 model properties to 0x10000
09 ;-----
10
11 DATA SEGMENT
12 P_A EQU 00H
13 P_B EQU 02H
14 P_C EQU 04H
15 CONNECT EQU 06H
16 DATA ENDS
17
18 CODE SEGMENT
19 ASSUME CS:CODE
20 ASSUME DS:CODE
21 ASSUME ES:CODE
22 ASSUME SS:CODE
23
24 ORG 0000H ;
25 MOV AX, DATA
26 MOV DS, AX
27 MOV AL, 10000000B ;
28 OUT CONNECT, AL
29
30 MAIN_LOOP:
31 ; HUNDREADTH POSITIONAL DATA
32 MOV AL, 11000000B
33 OUT P_A, AL
34 ; TENTH POSITIONAL DATA
35 MOV AL, 10110000B
36 OUT P_B, AL
37 ; UNIT POSITIONAL DATA
38 MOV AL, 10000000B
39 OUT P_C, AL ; Output data
40
41 JMP MAIN_LOOP
42 CODE ENDS
43 END ;
```

step 3: To display the result, the code was copy pasted to “source code section”. and on running the code, the following out put was obtained

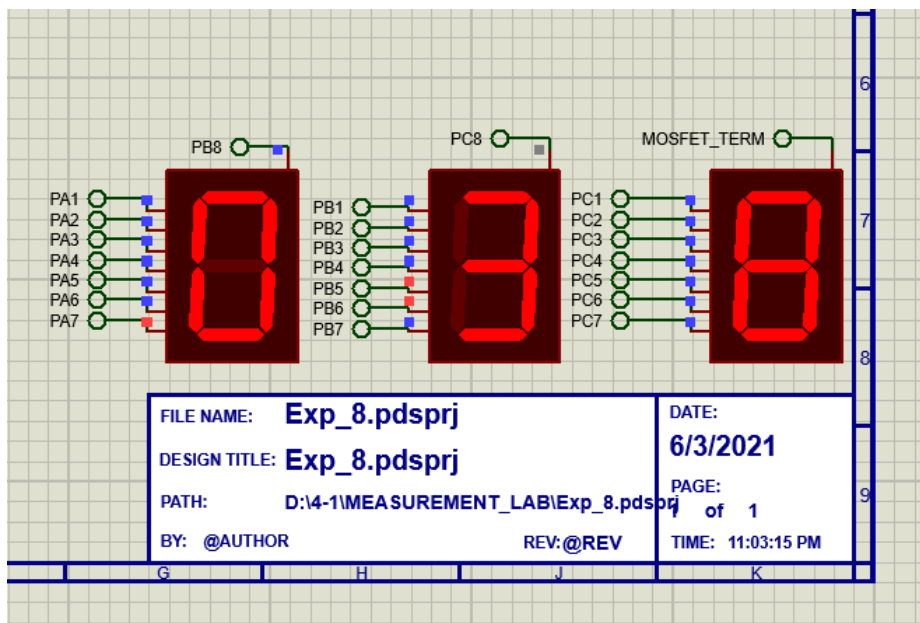


Figure 3 Output